

School of Computing Science and Engineering

B.Tech CSE
ETE - Jun 2023

Time : 3 Hours

Marks : 100

Sem II - G2UC101B / BEE01T1005

Introduction of Digital System

Your answer should be specific to the question asked

Draw neat labeled diagrams wherever necessary

1. Differentiate between
(a) a latch & a flipflop. K3 CO2 (5)
(b) T flipflop & D flipflop.
2. (a) Differentiate Signed Binary number and Unsigned Binary number? K1 CO1 (5)
(b) Represent +127 and -127 using 8-bit 1's complement form.
3. Convert $(A+B).(A+C).(B+C')$ into standard POS form. K2 CO1 (5)
4. (a) Simplify the boolean expression $Y = (A + B). (A'C' + C). (B'+AC)'$. K4 CO3 (10)
(b) Realize $Y = (A + B + C + D)'$ using 2-input NOR gates only.

OR

- Draw the circuit using logic gates of a T-type flip-flop. Draw its symbol and write its truth table. K4 CO3 (10)
5. (a) Convert Octal (1745) to hexadecimal. K1 CO1 (10)
(b) With neat sketch, realize the expression $Y = AB + CD$ by NAND gates only.
(c) Convert the Octal number (1072) to decimal.
 6. Explain the operation of SR latch using NAND & NOR gate. K4 CO3 (10)
 7. Draw and explain the truth table, boolean expression and circuit diagram of a BCD adder. K2 CO1 (10)
 8. Consider the SOP equation $x = A'BC'D + A'BCD' + AB'CD' + AB'CD + ABC'D' = ABC'D + ABCD'$. K3 CO2 (15)
(a) Use a K-map to produce the simplest SOP solution.
(b) How can you represent the above equation using XOR gates in combination with other gates? Draw a circuit diagram of your solution using XOR gates.
 9. Minimize the four-variable logic function using K-Map, $f(A, B, C, D) = \sum m(1,2,6,7,8,13,14,15) + d(3,5,12)$. K4 CO3 (15)
Make a K-map for the function, $f(A, B, C, D) = M(3,4,5,7,11,13,15) + d(6,8,10,12)$.

OR

- Design a Binary to Gray code converter. Represent the decimal number 4096 in Gray code. K4 CO4 (15)
10. (a) Simplify the expression $z = (B+BC) (B+B'C) (B+D)$ K3 CO2 (15)
(b) Design a logic circuit that will allow a signal to pass to the output only when control inputs B & C are both HIGH, otherwise, the output will stay LOW.