

Diploma in Engineering
Diploma in Electrical Engineering
ETE - Jun 2023

Time : 3 Hours

Marks : 100

Sem IV - N1DI403B - Electronics Engg-II

Your answer should be specific to the question asked

Draw neat labeled diagrams wherever necessary

- | | | |
|----|---|-------------|
| 1. | Illustrate types of encoders with their diagrams. | K2 CO2 (5) |
| 2. | Describe the Logic gates with symbols. | K2 CO2 (5) |
| 3. | Explain the half-adder and draw its K-Map. | K2 CO2 (5) |
| 4. | Describe the Full Adder with the help of its truth table and K-Map. | K2 CO2 (10) |
| 5. | Write the specifications of an OPAMP. | K3 CO3 (10) |
| 6) | Sketch the functional block diagram with the explanation of the function of its various blocks of 8085 microprocessors. | K4 CO4 (10) |

OR

- | | | |
|----|---|-------------|
| | Outline the need of microprocessor in modern technology. | K4 CO4 (10) |
| 7. | Show the diagram of an OPAMP circuit and explain its blocks. | K3 CO3 (10) |
| 8) | Consider modulation and demodulation and then mention its need in a communication system. | K5 CO5 (15) |

OR

- | | | |
|-----|---|-------------|
| | Recommend the necessary elements of a communication system. | K5 CO5 (15) |
| 9. | Outline the applications, advantages and disadvantages of 8085 microprocessor. | K4 CO4 (15) |
| 10. | Consider the advantages and disadvantages of satellite communication and explain. | K5 CO5 (15) |