

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**School of University Polytechnic****Diploma in Electrical Engineering  
Mid Term Examination - Nov 2023****Duration : 90 Minutes  
Max Marks : 50****Sem III - N1DI303B - Basic Electronics Engineering**General Instructions*Answer to the specific question asked**Draw neat, labelled diagrams wherever necessary**Approved data hand books are allowed subject to verification by the Invigilator*

- 1) Explain drift current and diffusion current in a PN junction. K2 (2)
- 2) What is a half adder circuit? K1 (3)
- 3) Explain is the breakdown mechanism. K2 (4)
- 4) Explain how a half adder can be implemented using basic logic gates. K2 (6)
- 5) Make use of the binary number system and explain its importance in computing. K3 (6)
- 6) Describe the operation of a 3-to-8 decoder using a truth table. K3 (9)
- 7) Analyze logic gates and their role in digital circuits. K4 (8)
  
- 8) Analyze the concept of virtual ground in op-amp circuits. K4 (12)

**OR**

- Analyze the control unit of a microprocessor work. K4 (12)