

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

School of Computing Science and Engineering

Bachelor of Computer Applications

Mid Term Examination - Nov 2023

Duration : 90 Minutes

Max Marks : 50

Sem I - E1UA108B - Electronics Workshop

General Instructions

Answer to the specific question asked


Draw neat, labelled diagrams wherever necessary

Approved data hand books are allowed subject to verification by the Invigilator


- 1) An Electric iron is rated 1000W, 240V. Find the current drawn & resistance of the heating element. K2 (2)
- 2) Why are resistors color-coded? K1 (3)
- 3) List out the characteristics of passive and active components. K2 (4)
- 4) Define node, junction, loop, mesh, branch with suitable examples. K2 (6)
- 5) The following circuit has resistors R1 and R2 connected in series. The resistance values are 5 Ω and 10 Ω respectively. If the voltage across R1 is 4 V, calculate the current through R2 and across the same resistor. K3 (6)
- 6) (i) If the input power to the rectifier is 150 W and output power is 50 W, then what will be the rectifier efficiency of the half-wave rectifier? K3 (9)
(ii) Differentiate between mesh and loop. (iii) Differentiate between node and junction.

- 7) (i) Find the total resistance of the three resistors connected in parallel.


K4 (8)

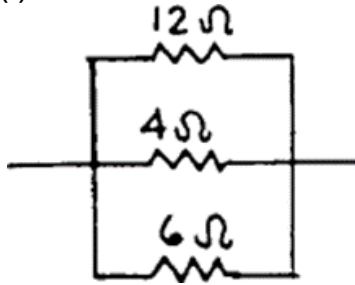

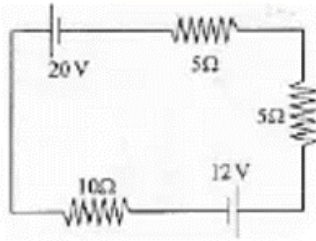- (ii) Determine the electric current that flows in the circuit as shown in the figure below.



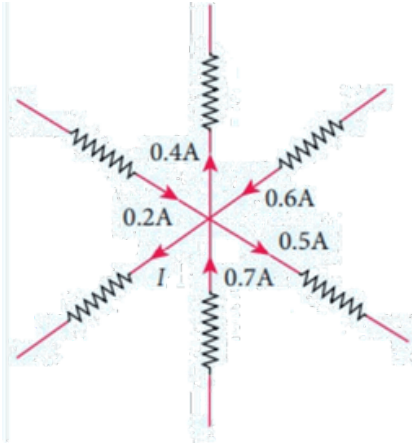- (iii) From the given circuit find the value of I



- 8) What is a rectifier? Draw neat waveforms for half wave rectifier and full wave rectifier.

K4 (12)

OR

Distinguish between zener and avalanche breakdown.

K4 (12)