


School of Engineering
B.TECH Electronics and Communication Engineering
Mid Term Examination - Nov 2023

Duration : 90 Minutes
Max Marks : 50


Sem III - G2UB301B - Network Analysis and Synthesis

General Instructions
 Answer to the specific question asked
 Draw neat, labelled diagrams wherever necessary
 Approved data hand books are allowed subject to verification by the Invigilator

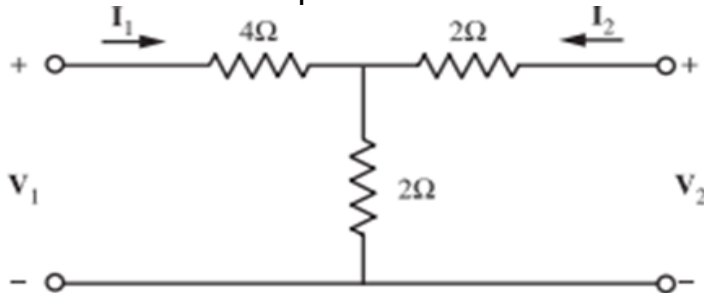- 1) How do you analyze an electrical circuit? K2 (2)
- 2) Define star -delta conversion and explain it with examples. K1 (3)
- 3) Explain linear and non linear network with example. K2 (4)
- 4) Illustrate concept of Tellegens theorem with applications. K2 (6)
- 5) Identify dual networks with example. K3 (6)
- 6) Solve the admittance parameters of T network as shown in figure. K3 (9)



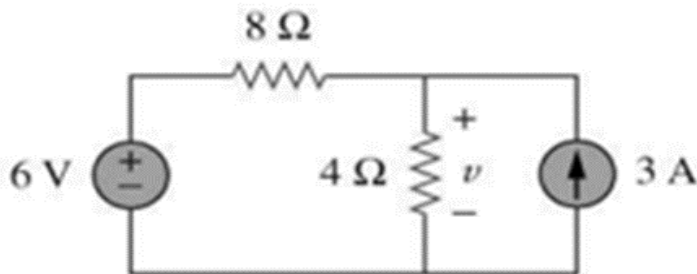- 7) Simplify voltage across 4 ohm resistor using superposition theorem . K4 (8)



- 8) Examine conversion of y parameter to z parameter. K4 (12)

OR

- Examine driving point impedance and admittance. K4 (12)