

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

School of Engineering**B.TECH Electrical Engineering
Mid Term Examination - Nov 2023****Duration : 90 Minutes
Max Marks : 50****Sem V - G2UB503C - Power Electronics**General Instructions*Answer to the specific question asked**Draw neat, labelled diagrams wherever necessary**Approved data hand books are allowed subject to verification by the Invigilator*

- 1) Compare the different power electronic switches. K2 (2)
- 2) Define duty cycle. K1 (3)
- 3) Explain the principle of chopper operation. K2 (4)
- 4) Illustrate the types of power transistors. K2 (6)
- 5) Model a step-down chopper circuit. K3 (6)
- 6) Develop differences between holding current and latching current in an SCR. K3 (9)
- 7) Classify the power electronic converters into different types. K4 (8)
- 8) Analyse the features of MOSFET and BJT. K4 (12)

OR

Analyse how a dual converter using two full converters give four quadrant operation. K4 (12)