

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

School of University Polytechnic

Diploma in Electrical Engineering
Mid Term Examination - May 2024

Duration : 90 Minutes
Max Marks : 50

Sem II - N1DI202B - Basic Electrical EnggGeneral Instructions

Answer to the specific question asked

Draw neat, labelled diagrams wherever necessary

Approved data hand books are allowed subject to verification by the Invigilator

- 1) Explain the application of ohms law. K2 (2)
- 2) Define the heating effect of electric current. K1 (3)
- 3) Explain the effect of temperature on resistance. K2 (4)
- 4) Explain Kirchhoff's current laws. K2 (6)
- 5) Illustrate and find the total resistance, current and voltage across each resistor in given circuit. K3 (6)
- 6) Illustrate the series combination of resistance. K3 (9)
- 7) Compare Thevenin's theorem and Norton's theorem. K4 (8)

- 8) Analyze Norton's theorem with example. K4 (12)

OR

Compare and contrast the graphical representations of ideal and practical current sources, emphasizing their differences. K4 (12)