

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

School of Computing Science and Engineering

Bachelor of Technology in Computer Science and Engineering

Mid Term Examination - May 2024

Duration : 90 Minutes

Max Marks : 50

Sem II - G2UC101B - Introduction to Digital SystemGeneral Instructions*Answer to the specific question asked**Draw neat, labelled diagrams wherever necessary**Approved data hand books are allowed subject to verification by the Invigilator*

- 1) What are the methods adopted to reduce Boolean function? K2 (2)
- 2) What is the concept of Boolean duality? K1 (3)
- 3) What do you mean by don't care conditions? Give an example. K2 (4)
- 4) Subtract (9) from (4), Using 2's complement method. K2 (6)
- 5) What do you mean by XNOR logic? Draw its truth table and write its boolean expression. K3 (6)
- 6) Design a logic circuit that has three inputs, A,B and C, and whose output will be HIGH when a majority of the inputs are HIGH. K3 (9)
- 7) Applying the principles of Boolean algebra, analyze the given Boolean expression, $F(X, Y, Z) = X'Y + YZ' + YZ + XY'Z$. K4 (8)
- 8) Reduce the expression $\Sigma m(0,2,3,4,5,6)$ using mapping and implement it in NAND logic. K4 (12)

OR

- Make a K-map for the function $f = AB + AC' + C + AD + AB'C + ABC$. (b) K4 (12)
Express 'f' in standard SOP form.