

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

**School of Engineering****B.TECH Electrical Engineering  
Mid Term Examination - May 2024****Duration : 90 Minutes  
Max Marks : 50****Sem IV - G2UB405C - Electrical Measurement and Instrumentation**General Instructions*Answer to the specific question asked**Draw neat, labelled diagrams wherever necessary**Approved data hand books are allowed subject to verification by the Invigilator*

- 1) Compare analog and digital instruments. K2 (2)
- 2) Define repulsive type moving iron instrument. K1 (3)
- 3) Explain the term Accuracy, Precision, Resolution and Thrashold. K2 (4)
- 4) Illustrate the the concept of current transformer K2 (6)
- 5) What are the applications of wheat stone bridge and explain its limitations? K3 (6)
- 6) Construct the circuit diagram of various types of ohmmeter also compare them. K3 (9)
- 7) Classify with the help of cicuit diagram, rectifier type instrument on the basis of their application. Also specify merits and demerits. K4 (8)
- 8) Examine the bridge balance condition for the Schering bridge with the help of necessary circuit diagram. K4 (12)

**OR**

- Explain construction and working of Owen bridge. K4 (12)