

**School of Biomedical Science****B.Tech Biotechnology  
Semester End Examination - Jul 2024****Duration : 180 Minutes  
Max Marks : 100****Sem II - G2UC101B - BEE01T1005 Introduction to Digital System - 1**General Instructions*Answer to the specific question asked**Draw neat, labelled diagrams wherever necessary**Approved data hand books are allowed subject to verification by the Invigilator*

- 1) Differentiate Signed Binary number and Unsigned Binary number. K1(2)
- 2) Explain Binary Full adder circuit. K2(4)
- 3) Construt 3 to 8 line decoder with necessary diagram. K2(6)
- 4) Design a Gray-to-Binary code converter. K3(9)
- 5) Discuss a combinational circuits to convert binary coded decimal number into an excess-3 code K3(9)
- 6) Design a T flip-flop using JK flip-flop. K5(10)
- 7) Design a combinational circuit that converts a 4-bit binary number number to 4-bit gray code. K4(12)
- 8) Minimize the following boolean function- $F(A, B, C, D) = \sum m(1,3,5,7,8,9,12,13) + \sum d(14,15)$ . Write the procedure to expand an SOP expression into stanadard SOP form. K5(15)
- 9) Minimize the following boolean function- $F(A, B, C, D) = \sum m(1, 2,3,5,7,8,9) + \sum d(12,14)$ . Write the procedure to expand an POS expression into stanadard POS form. K5(15)
- 10) Obtain the minimal SOP expression for  $\sum m(2,3,5,7,9,11,12,13,14,15)$  and implement it in NAND logic. K6(18)