

School of University Polytechnic

**Diploma in Electrical Engineering
Semester End Examination - Jul 2024**

**Duration : 180 Minutes
Max Marks : 100**

Sem II - N1DI202B - Basic Electrical Engg*General Instructions*

Answer to the specific question asked

Draw neat, labelled diagrams wherever necessary

Approved data hand books are allowed subject to verification by the Invigilator

- | | | |
|-----|--|--------|
| 1) | Define resistance and its types. | K1(2) |
| 2) | Explain the concepts of step-up transformers. | K2(4) |
| 3) | Explain the concepts of the voltage source and the current source. | K2(6) |
| 4) | Illustrate the electro-magnetic field produced by the flow of electric current. | K3(9) |
| 5) | Illustrate the working principle of an auto-transformer and its applications. | K3(9) |
| 6) | Examine how a transformer operates and its importance in electrical systems. | K5(10) |
| 7) | Analyze the features of DC generators and their applications. | K4(12) |
| 8) | Examine Kirchhoff's laws Are they applicable to both a.c. and d.c. circuits | K5(15) |
| 9) | Analyze how the concepts of voltage, current, resistance, and conductance in electric circuits relate to the concepts of MMF, flux, reluctance, and permeability in magnetic circuits. | K5(15) |
| 10) | Discuss the concept of current growth, decay, and time constant in an inductive (RL) circuit, including mathematical expressions. | K6(18) |