

**School of University Polytechnic****Diploma in Electrical Engineering  
Semester End Examination - Jul 2024****Duration : 180 Minutes  
Max Marks : 100****Sem III - N1DI303B - Basic Electronics Engineering**General Instructions*Answer to the specific question asked**Draw neat, labelled diagrams wherever necessary**Approved data hand books are allowed subject to verification by the Invigilator*

- |     |  |        |
|-----|--|--------|
| 1)  | What is a PN junction?   | K1(2)  |
| 2)  | Describe combinational circuit.  | K2(4)  |
| 3)  | Explain the operation of an op-amp adder circuit.  | K2(6)  |
| 4)  | Compute the concept of a scale changer using an op-amp.  | K3(9)  |
| 5)  | Carryout the display devices.  | K3(9)  |
| 6)  | Determine the pin diagram of 8085 microprocessor and explain.  | K5(10) |
| 7)  | sketch the 4 is to 1 multiplexer.  | K4(12) |
| 8)  | Determine the maximum value of the AC voltage required at the input. A halfwave rectifier is utilized to supply 20 volt dc to a resistive load of 400 ohm. The diode used in halfwave resctifier has a forward resistance of 40 ohm. | K5(15) |
| 9)  | Defend the primary purpose of using op-amp configurations like inverting and non-inverting amplifiers.   | K5(15) |
| 10) | Discuss how a full adder can be implemented using multiple half adders.  | K6(18) |