

## School of Engineering

**B.TECH Electronics and Communication Engineering  
Semester End Examination - Jul 2024**

**Duration : 180 Minutes  
Max Marks : 100**

### Sem III - G2UB301B/ BTEE2002 - Network Analysis and Synthesis


General Instructions

*Answer to the specific question asked*


*Draw neat, labelled diagrams wherever necessary*

*Approved data hand books are allowed subject to verification by the Invigilator*

- |    |  |       |
|----|--|-------|
| 1) | Compare bilateral and unilateral network.  | K1(2) |
| 2) | Explain concept of network function in network analysis.                                     | K2(4) |
| 3) | Illustrate the concept of source transformation.   | K2(6) |
| 4) | <b>Solve all branch currents and the voltage across the 5 ohm resistor by node analysis.</b> | K3(9) |

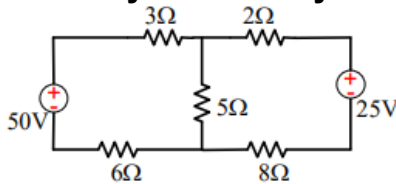

- |    |  |       |
|----|--|-------|
| 5) | For the circuit shown in Fig below, determine Norton's equivalent circuit between the output terminals, AB | K3(9) |
|----|--|-------|

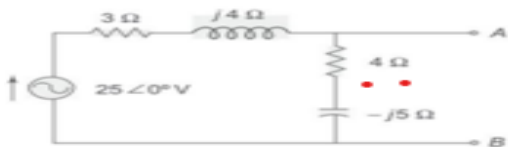

- |    |  |        |
|----|--|--------|
| 6) | The h parameters of the two port are given .Compute Y and ABCD parameters. | K5(10) |
|----|--|--------|

$$h = \begin{bmatrix} 5 & 2 \\ 3 & 6 \end{bmatrix}$$

- |    |  |        |
|----|--|--------|
| 7) | Examine how Norton's theorem similar to Thevenin's theorem ? In what respect do they differ? | K4(12) |
| 8) | Measure given transfer function.in s -plane $f(s) = (s+5)/(s+4)(s+3)$                        | K5(15) |
| 9) | A current source of 5A having an internal resistance of 10Ω is                               | K5(15) |

connected to a load resistor of  $5\Omega$ . Find the current in the load resistor using source transformation .

10) Derive star to delta conversion.

K6(18)