 


Name. _____		Printed Pages:01		
Student Admn. No.: _____				
School of basic Science Summer Term Examination – July - August 2024 [Programme: B.Sc] [Semester: VI] [Batch: All]				
Course Title: Analog and Digital Principles and Applications			Max Marks: 100	
Course Code: CIUD604B			Time: 3 Hrs.	
Instructions:		1. All questions are compulsory. 2. Assume missing data suitably, if any.		
		K Level	COs	Marks
SECTION-A (15 Marks)		5 Marks each		
1.	Discuss the construction and working of JFET.	KL1	CO2	5
2.	a) What is 2's complement of the number 1101101? b) Add -5 and -4 using 2's complement.	KL1	CO3	5
3.	Find the expression for output 	KL2	CO4	5
SECTION-B (40 Marks)		10 Marks each		
4.	What do u mean by universal gate? Draw the NAND gate using transistors and write the truth table	KL3	CO4	10
5.	Design a Full – Adder using two Half - Adder and OR gate, draw the Block diagram with logic circuit?	KL3	CO4	10
6.	Define built-in-potential (potential barrier). What will be direction of internal electric field developed due to potential barrier in a zero biased p-n junction diode?	KL4	CO1	10
7.	Using two port network, draw the h parameters for common base configuration and calculate the gain.	KL4	CO2	10
SECTION-C (45 Marks)		15 Marks each		
8.	Explain the truth table of half subtractor and design the half subtractor circuit using NOR gates?	KL5	CO4	15
9.	Estimate the resistance of an intrinsic Ge rod 1 mm long, 1 mm wide and 1 mm thick at 300 K. the intrinsic carrier density $2.5 \times 10^{19} \text{ m}^{-3}$ is at 300 K and the mobility of electron and hole are 0.39 and $0.19 \text{ m}^2 \text{ v}^{-1} \text{ s}^{-1}$.	KL5	CO1	15
10	In SR flip flop describe the (a) circuit diagram using NAND gates; (b) truth table; (c) logic symbol; (d) find out the Boolean equation using K-map.	KL5	CO4	15