

UNIT 4

Two Port Networks


GALGOTIAS
UNIVERSITY

Contents

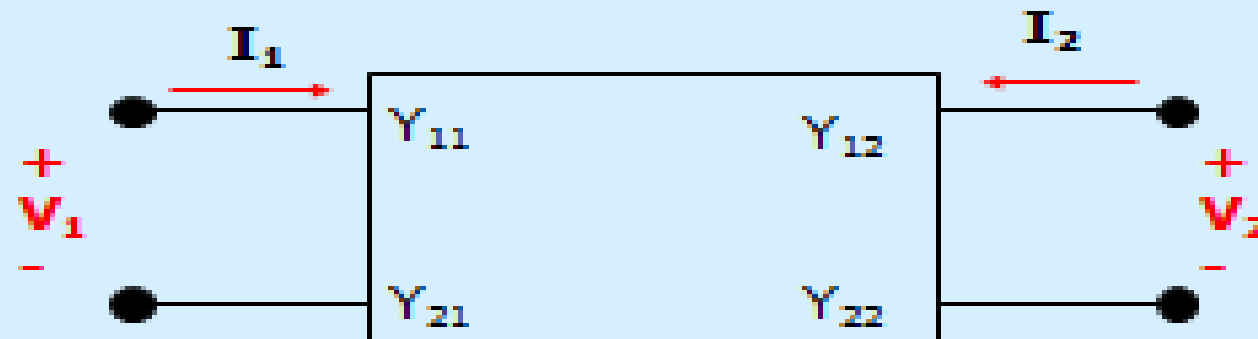1. Introduction to two port networks
2. Z –Parameters
3. Y- Parameters
4. ABCD – Parameters
5. Inverse ABCD – Parameters
6. h-Parameters
7. Inverse h-Parameters
8. Condition for reciprocity
9. Condition for symmetry
10. Inter-relationships between the parameters
11. Inter-connections of two port networks

Y - PARAMETER

- Y – parameter also called admittance parameter and the units is siemens (S).
- The “black box” that we want to replace with the Y-parameter is shown below.



- The terminal current can be expressed in term of terminal voltage as:

$$I_1 = y_{11}V_1 + y_{12}V_2 \quad \text{———— (1)}$$

$$I_2 = y_{21}V_1 + y_{22}V_2 \quad \text{———— (2)}$$

- In matrix form:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- The y-parameter that we want to determine are Y_{11} , Y_{12} , Y_{21} , Y_{22} . The values of the parameters can be evaluate by setting:
 - i) $V_1 = 0$ (input port short – circuited).
 - ii) $V_2 = 0$ (output port short – circuited).

- Thus;

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$


$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$



T (ABCD) PARAMETER

- T – parameter or ABCD – parameter is a another set of parameters relates the variables at the input port to those at the output port.
- T – parameter also called *transmission parameters* because this parameter are useful in the analysis of transmission lines because they express sending – end variables (V_1 and I_1) in terms of the receiving – end variables (V_2 and $-I_2$).

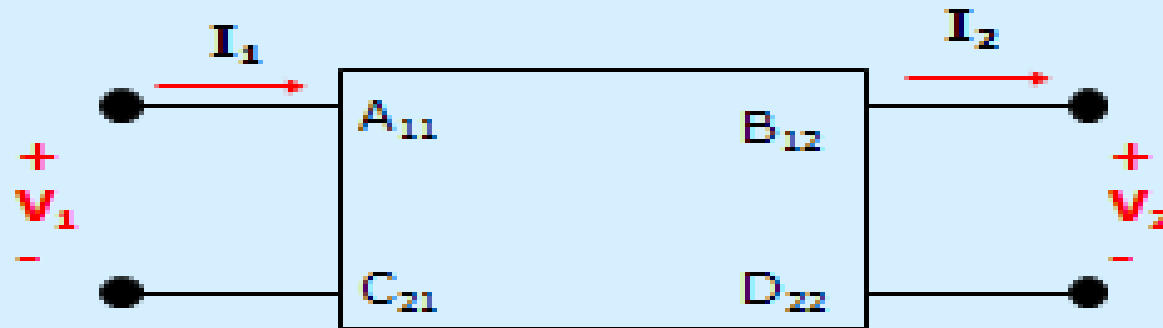- The “black box” that we want to replace with T – parameter is as shown below.



- The equation is:

$$V_1 = AV_2 - BI_2 \dots \dots (1)$$

$$I_1 = CV_2 - DI_2 \dots \dots (2)$$

- In matrix form is:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

- The T – parameter that we want determine are A, B, C and D where A and D are dimensionless, B is in ohm (Ω) and C is in siemens (S).
- The values can be evaluated by setting
 - i) $I_2 = 0$ (input port open – circuit)
 - ii) $V_2 = 0$ (output port short circuit)

- Thus;

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

- In term of the transmission parameter, a network is reciprocal if;

$$\boxed{AD - BC = 1}$$

Summary

- A two-port network has an input port and an output port, each with each port involving a single current and a single voltage.
- If the two-port network is linear and does not contain any independent sources, it may be possible to characterize up to 6 different sets of matrix relationships. We discussed four: admittance $[y]$, impedance $[z]$, hybrid $[h]$, and transmission $[T]$. If the parameters exist, they can be calculated or measured individually by short-circuiting or open-circuiting the appropriate port.
- A two-port network is reciprocal if $y_{12}=y_{21}$, $z_{12}=z_{21}$, $h_{12}=-h_{21}$. If the linear network only contains passive elements, it is reciprocal.
- When two-port networks are connected (a) in series, their impedance parameters add; (b) in parallel, their admittance parameters add; and (c) in cascade, their transmission parameters multiply.

References

1. M. E. Van Valkenburg, "Network Analysis", Prentice Hall, 2006.
2. D. Roy Choudhury, "Networks and Systems", New Age International Publications, 1998.
3. W. H. Hayt and J. E. Kemmerly, "Engineering Circuit Analysis", McGraw Hill Education, 2013.
4. C. K. Alexander and M. N. O. Sadiku, "Electric Circuits", McGraw Hill Education, 2004.
5. K. V. V. Murthy and M. S. Kamath, "Basic Circuit Analysis", Jaico Publishers, 1999. Syllabus
6. K.M. Soni, " Network Theory", S.K. Kataria Publication

