

The logo of Galgotias University is a stylized circular emblem with three curved, overlapping bands in shades of yellow, blue, and red, resembling a 'G' or a wave.

DC Motor Starters

GALGOTIAS
UNIVERSITY

Acknowledgement: The materials presented in this lecture has been taken from open source, reference books etc. This can be used only for student welfare and academic purpose.

Recap

- Needs of DC motors
- Back EMF in DC motor
- Classification of DC motor
- Torque in DC motor
- DC motor Characteristics
- Speed control of DC motor

GALGOTIAS
UNIVERSITY

Lecture-18 Objectives

- Starting of DC motor
- Swinburne's test
- Efficiency
- Application of DC motor

GALGOTIAS
UNIVERSITY

DC Motor Starters

Starting of DC motors – Necessity of Starters

- We know that in a DC motor, the back e.m.f.,

$$E_b = V - I_a R_a$$

$$\therefore I_a = \frac{V - E_b}{R_a}$$

- At starting, when the motor is stationary, back e.m.f. is zero.

$$\therefore I_a = \frac{V}{R_a}$$

- If the motor is directly switched on to the supply, the armature will draw a heavy current from the supply because of small armature resistance.

DC Motor Starters

Necessity of Starters – Example

- 5 H.P., 220 V shunt motor has a full-load current of 20 A and an armature resistance of about 0.5 ohms. If this motor is directly switched on to supply, it would take an armature current of $220/0.5 = 440$ A which is 22 times the full-load current.
- This high starting current may result in:
 - ✓ burning of armature due to excessive heating effect
 - ✓ damaging the commutator and brushes due to heavy sparking
 - ✓ excessive voltage drop in the line to which the motor is connected

DC Motor Starters

Control of Starting Current

- In order to avoid excessive current at starting, a variable resistance is inserted in series with the armature circuit.
- This resistance is gradually reduced as the motor gains speed and it is cut out completely when the motor has attained full speed.
- The value of starting resistance is generally such that starting current is limited to 1.25 to 2 times the full-load current.


DC Motor Starters

Control of Starting Current

- In order to avoid excessive current at starting, a variable resistance is inserted in series with the armature circuit.
- This resistance is gradually reduced as the motor gains speed and it is cut out completely when the motor has attained full speed.
- The value of starting resistance is generally such that starting current is limited to 1.25 to 2 times the full-load current.


DC Motor Starters

Two Point Starter

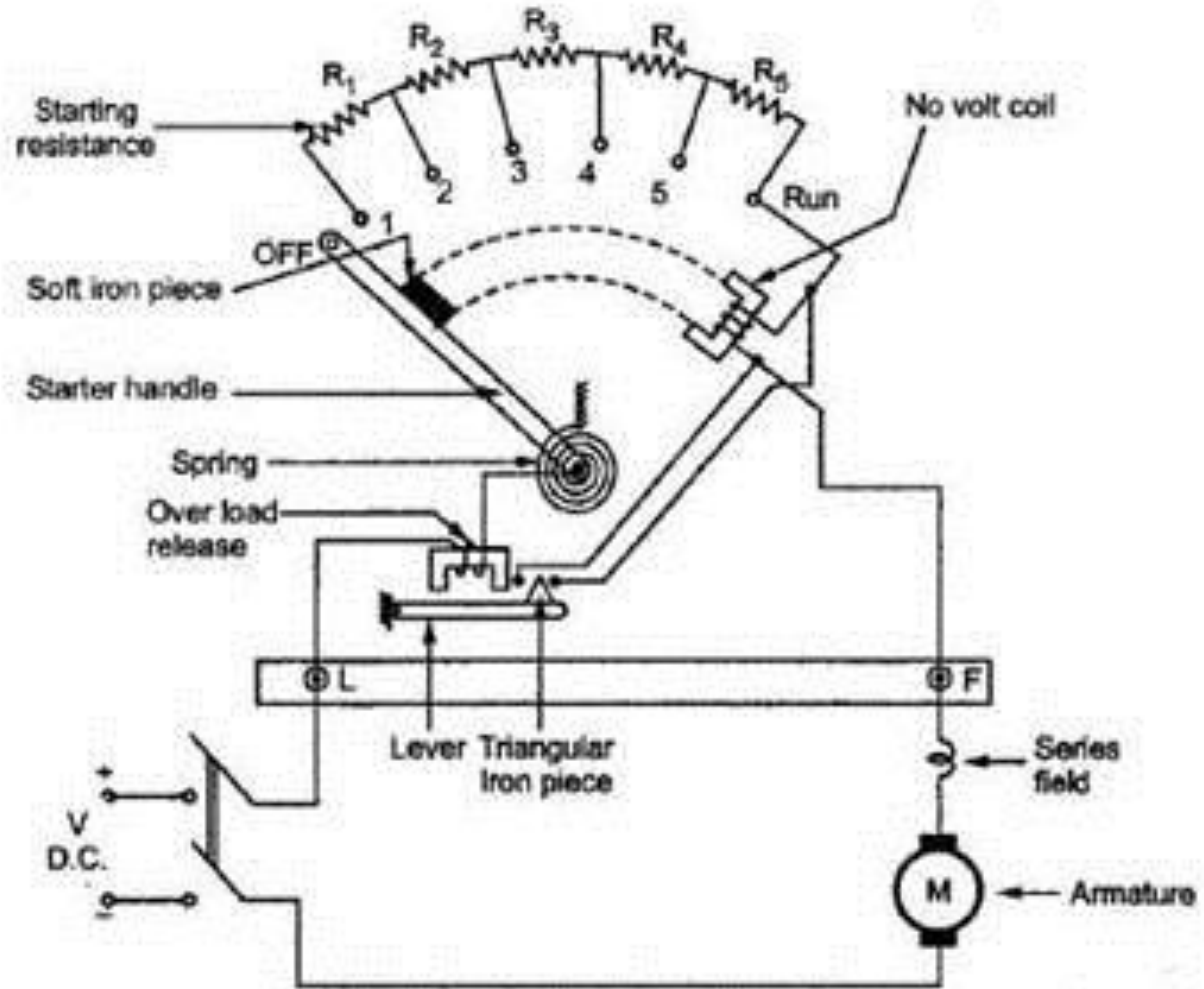

DC Motor Starters


Three Point Starter

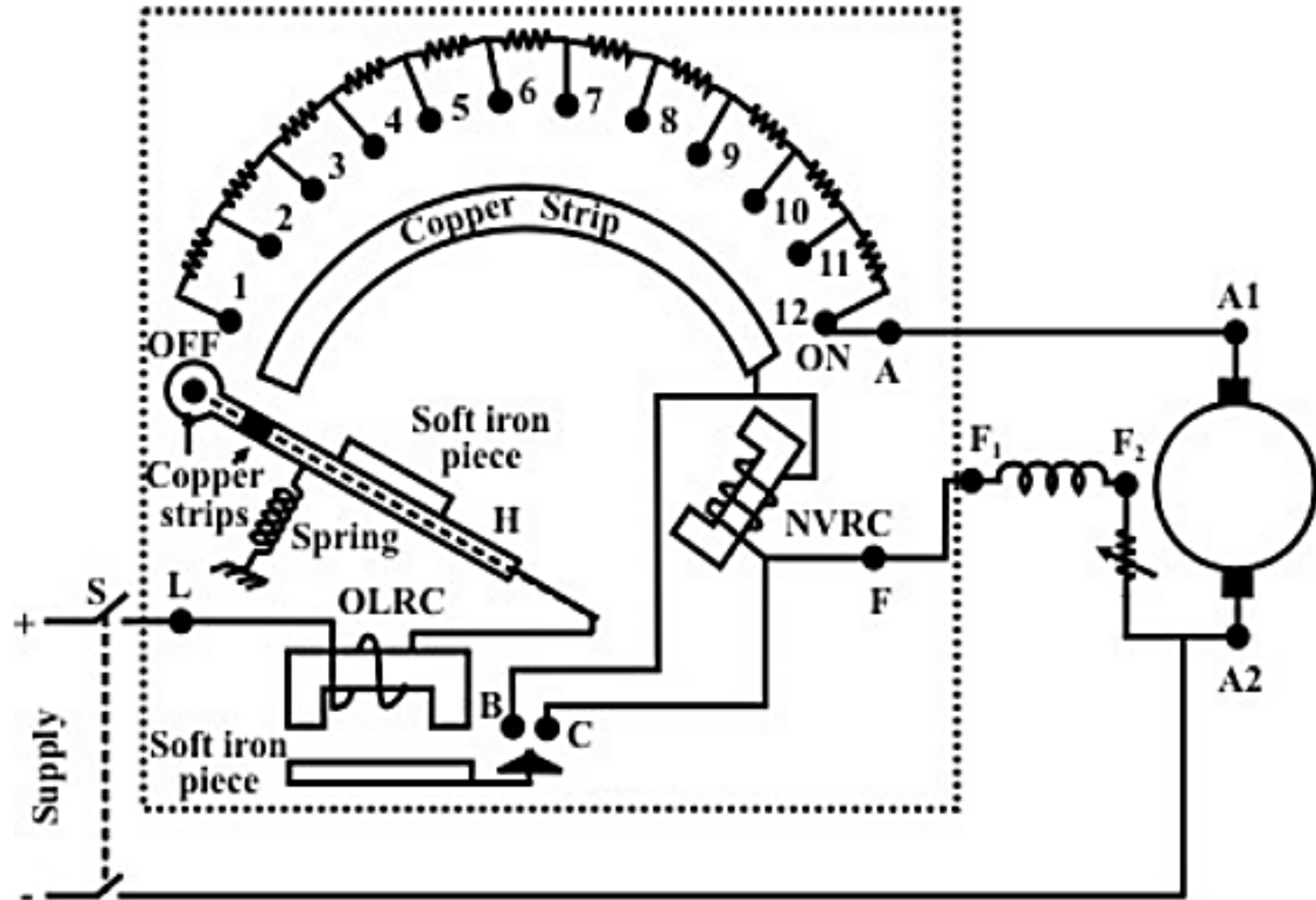

GA
UN

DC Motor Starters

Four Point Starter

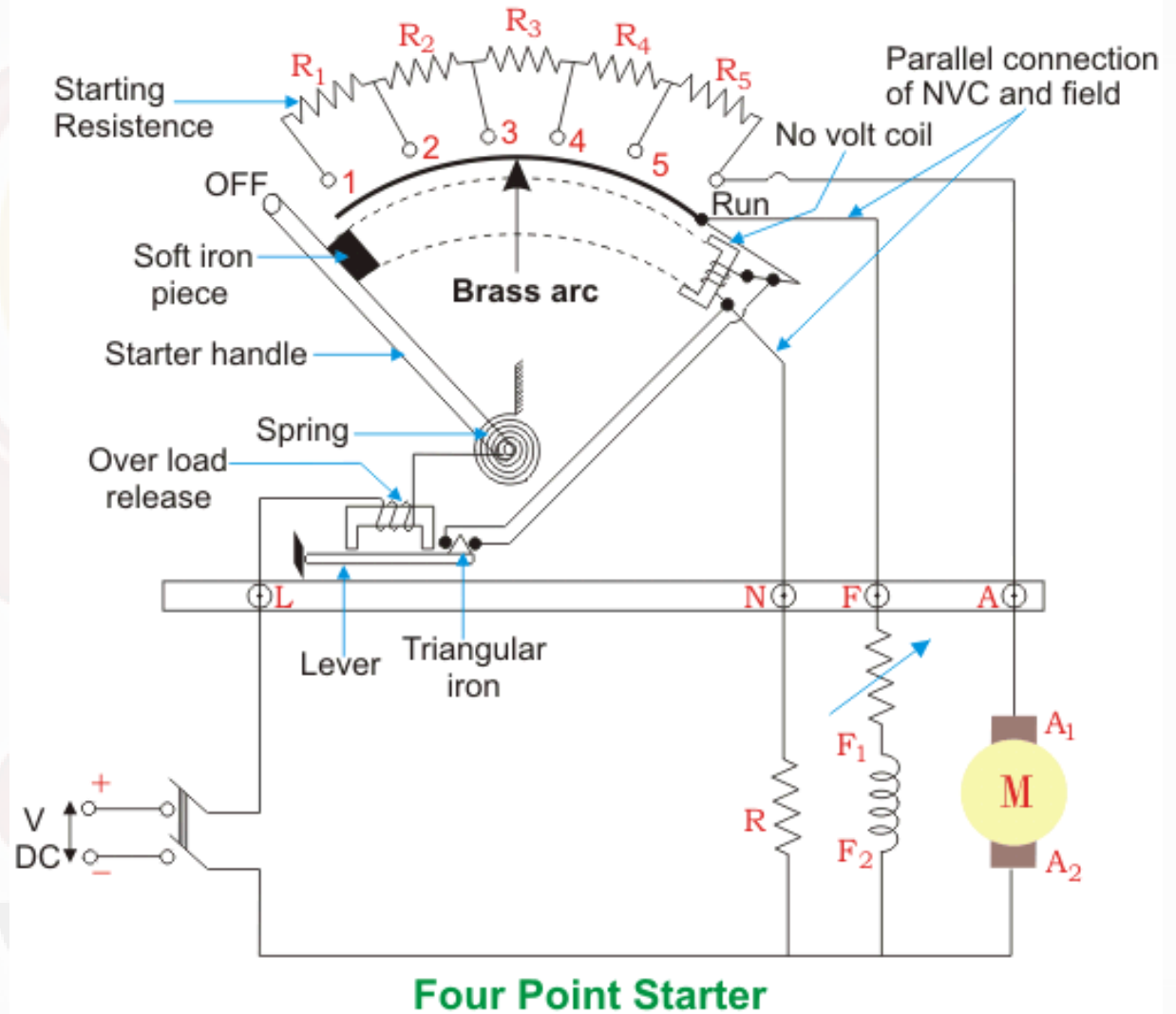

DC Motor Starters

Testing of DC Motor

- Brake test
- Swinburne's test
- Hopkinson's test
- Retardation test

GALGOTIAS
UNIVERSITY


DC Motor Starters

Swinburne's Test

- In this method, the d.c. machine (generator or motor) is run as a motor at no load and losses of the machine are determined.
- Once the losses of the machine are known, its efficiency at any desired load can be determined in advance.
- This method is applicable to those machines in which flux is practically constant at all loads e.g., shunt and compound machines.

DC Motor Starters

Swinburne's Test

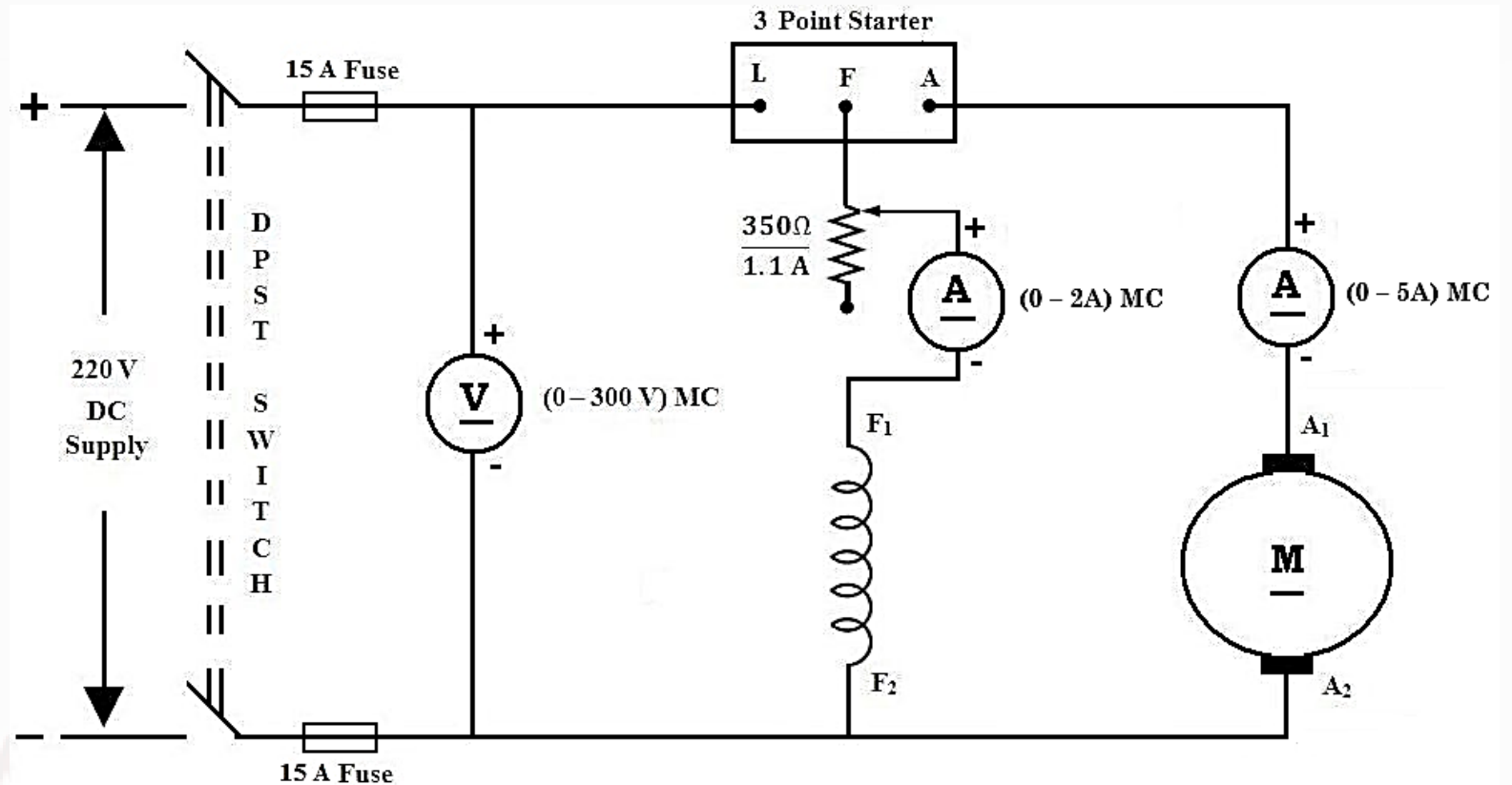

Data Observed

- Supply voltage $V = \underline{\hspace{2cm}}$ volts
- No load shunt field current $I_{sh} = \underline{\hspace{2cm}}$ amps
- No load armature current $I_{a0} = \underline{\hspace{2cm}}$ amps

DC Motor Starters

Swinburne's Test – Calculation of Constant Loss

Constant loss, $W_C = \text{Input to motor} - \text{Armature copper loss}$

$$\text{Line Current, } I_{L0} = I_{a0} + I_{sh}$$

$$\text{No load input to motor} = V \cdot I_{L0} = V \cdot (I_{a0} + I_{sh})$$

$$\text{Armature copper loss, } P_c = I_{a0}^2 \cdot R_a$$

$$W_C = V \cdot (I_{a0} + I_{sh}) - I_{a0}^2 \cdot R_a$$

DC Motor Starters

Efficiency of the Machine when Running as Motor

$$\text{Armature current, } I_a = I_L - I_{sh}$$

$$\text{Input power to motor, } P_i = V \cdot I_L$$

$$\text{Armature copper loss, } P_C = I_a^2 \cdot R_a = (I_L - I_{sh})^2 \cdot R_a$$

$$\text{Total losses, } P_T = \text{Armature copper loss} + \text{Constant loss}$$

$$\text{Output power, } P_O = \text{Input} - \text{Total losses} = P_i - P_T$$

$$\text{Output Power } P_O \text{ in HP} = \left(\frac{P_O \text{ in watts}}{735.5} \right)$$

DC Motor Starters

Applications of DC Motors

Shunt Motor:

- Blowers and fans
- Centrifugal and reciprocating pumps
- Lathe machines
- Machine tools
- Milling machines
- Drilling machines

GALGOTIAS
UNIVERSITY

DC Motor Starters

Applications of DC Motors

Series Motor:

- Cranes
- Hoists , Elevators
- Trolleys
- Conveyors
- Electric locomotives

GALGOTIAS
UNIVERSITY

DC Motor Starters

Applications of DC Motors

Compound Motor:

- Rolling mills
- Punches
- Shears
- Heavy planers
- Elevators

GALGOTIAS
UNIVERSITY

DC Motor Starters

Summary

- Starting of DC motor
- Swinburne's test
- Efficiency
- Application of DC motor

GALGOTIAS
UNIVERSITY