

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

TOPICS


SIGLE PHASE HALF BRIDGE INVERTERS

GALGOTIAS
UNIVERSITY

Name of the Faculty: Saravanan D

Program Name: B.Tech-EE/EEE

Single phase Half bridge Inverter

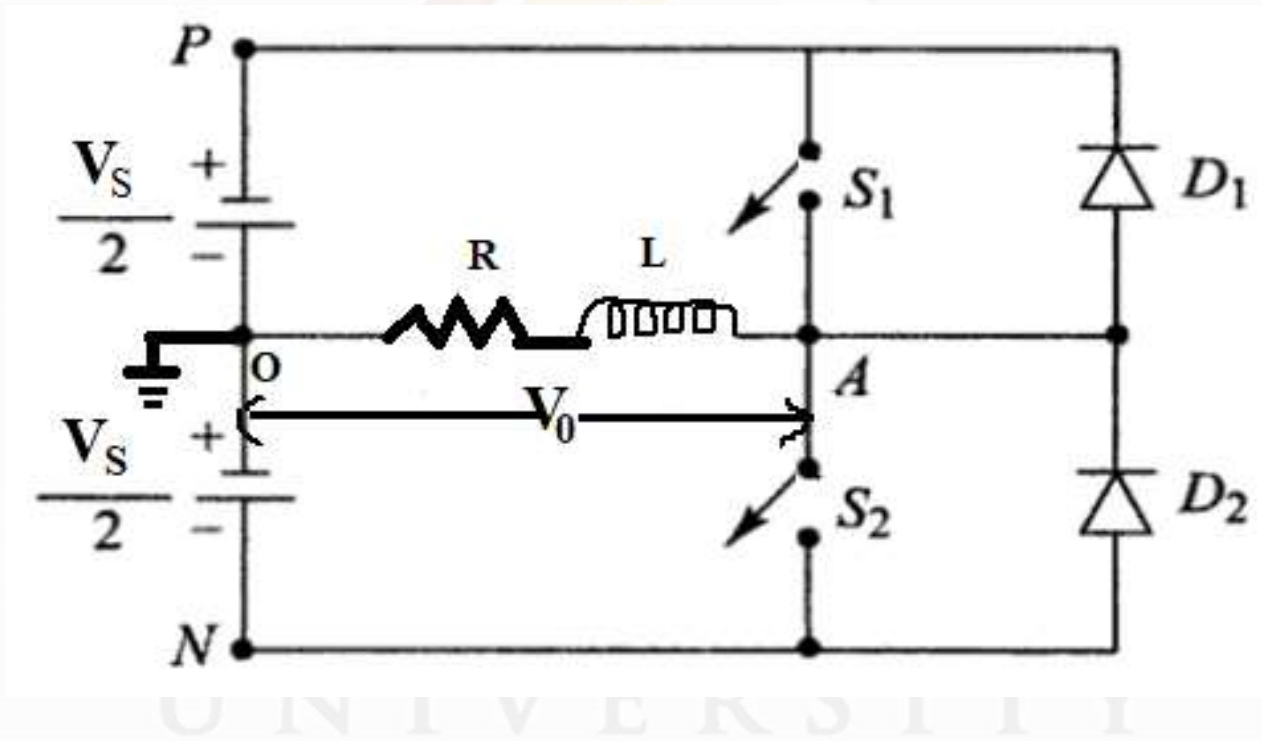


School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

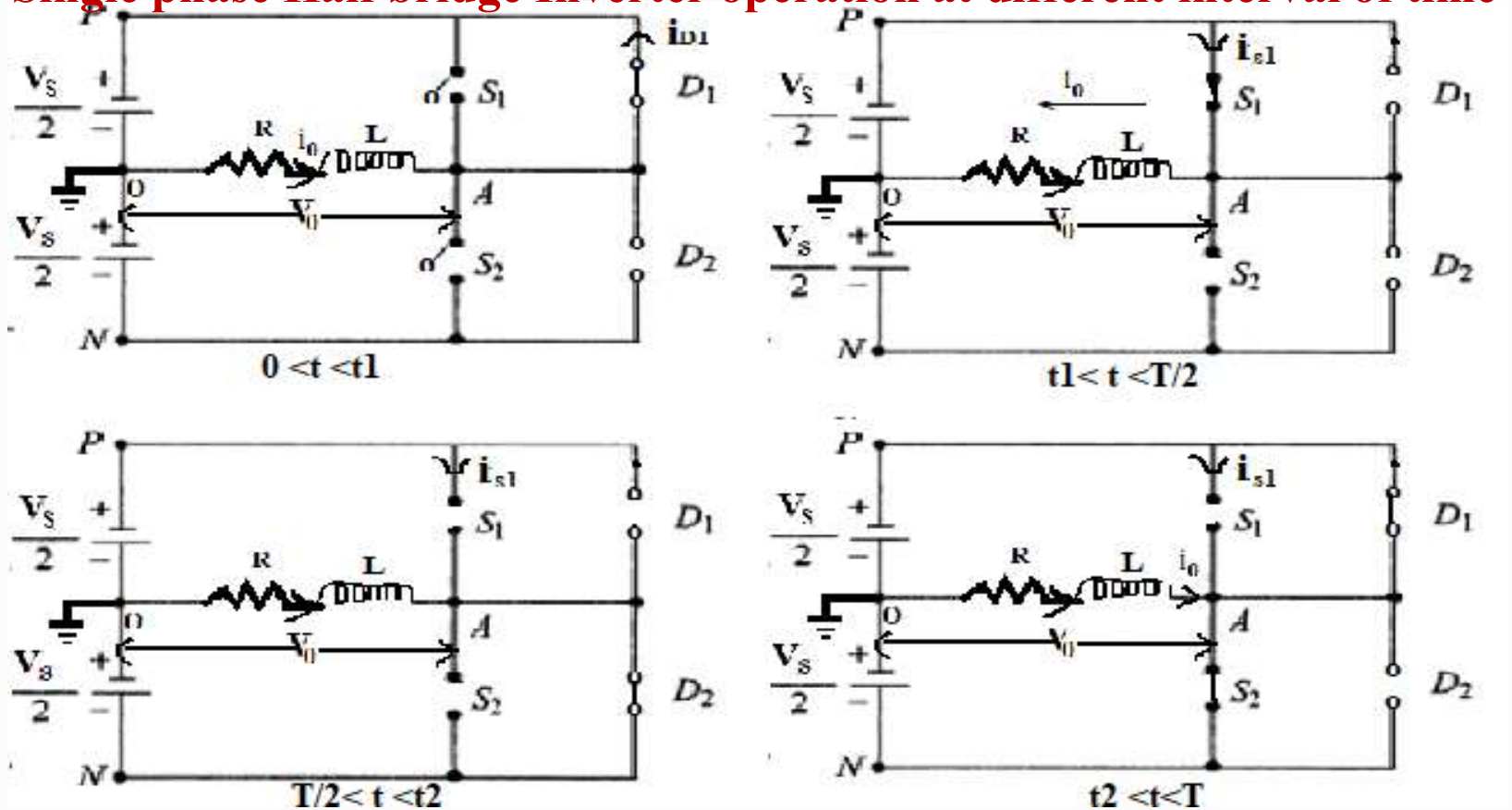Single phase Half bridge Inverter operation at different interval of time



Name of the Faculty: Saravanan D

Program Name: B.Tech-EE/EEE

Mode I($t_1 < t < t_2$):

S1 is turned-on at instant t_1 , the load voltage is equal to $+V_s/2$ and the positive load current increases gradually. At instant t_2 , the load-current reaches the peak value. Switch S1 is turned-off at this instant. Due to same-polarity of load voltage and load current, the energy is stored by the load.

Mode II($t_2 < t < t_3$):

Due to inductive-load, the load current direction will be maintained even-after S is turned-off. The self-induced voltage in the load will be negative. In this mode, the stored energy in load is fed back to the lower half of the source and the load voltage is clamped to $-V_s/2$

GALGOTIAS
UNIVERSITY

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

Mode III($t_3 < t < t_4$):

At instant t_3 , the load-current goes to zero, indicating that a_1 , the stored energy, has been returned back to the lower half of supply. At instant t_3 , S2 is turned-on. This will produce a negative load voltage $e_0 = -V_s/2$ and a negative load current. Load current reaches a negative peak at the end of this interval.

Mode IV($t_4 < t < t_5$):

Switch S2 is turned-off at instant t_4 . The self induced voltage in the inductive load will maintain the load current. The load voltage changes its polarity to become positive $V_s/2$, load current remains negative and the stored energy in the load is returned back to the upper half of the d.c source. At t_5 , the load current goes to 0 and S1 can be turned-on again. This cycle of operation repeats.

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

Summarization of the time intervals by switches and diodes

S.NO	Time Interval	Device Conduc ts	Output Voltage (V_0)	Output Curent (I_0)	Switch Current (i_{S1})	Switch Diode (i_{D1})
1	$0 < t < t_1$	D_1	$V_0 > 0$	$I_0 < 0$	0	$-I_0$
2	$t_1 < t < T/2$	S_1	$V_0 > 0$	$I_0 > 0$	I_0	0
3	$T/2 < t < t_2$	D_2	$V_0 < 0$	$I_0 > 0$	0	0
4	$t_2 < t < T$	S_2	$V_0 < 0$	$I_0 < 0$	0	0

GALGOTIAS
UNIVERSITY

Name of the Faculty: Saravanan D


Program Name: B.Tech-EE/EEE

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

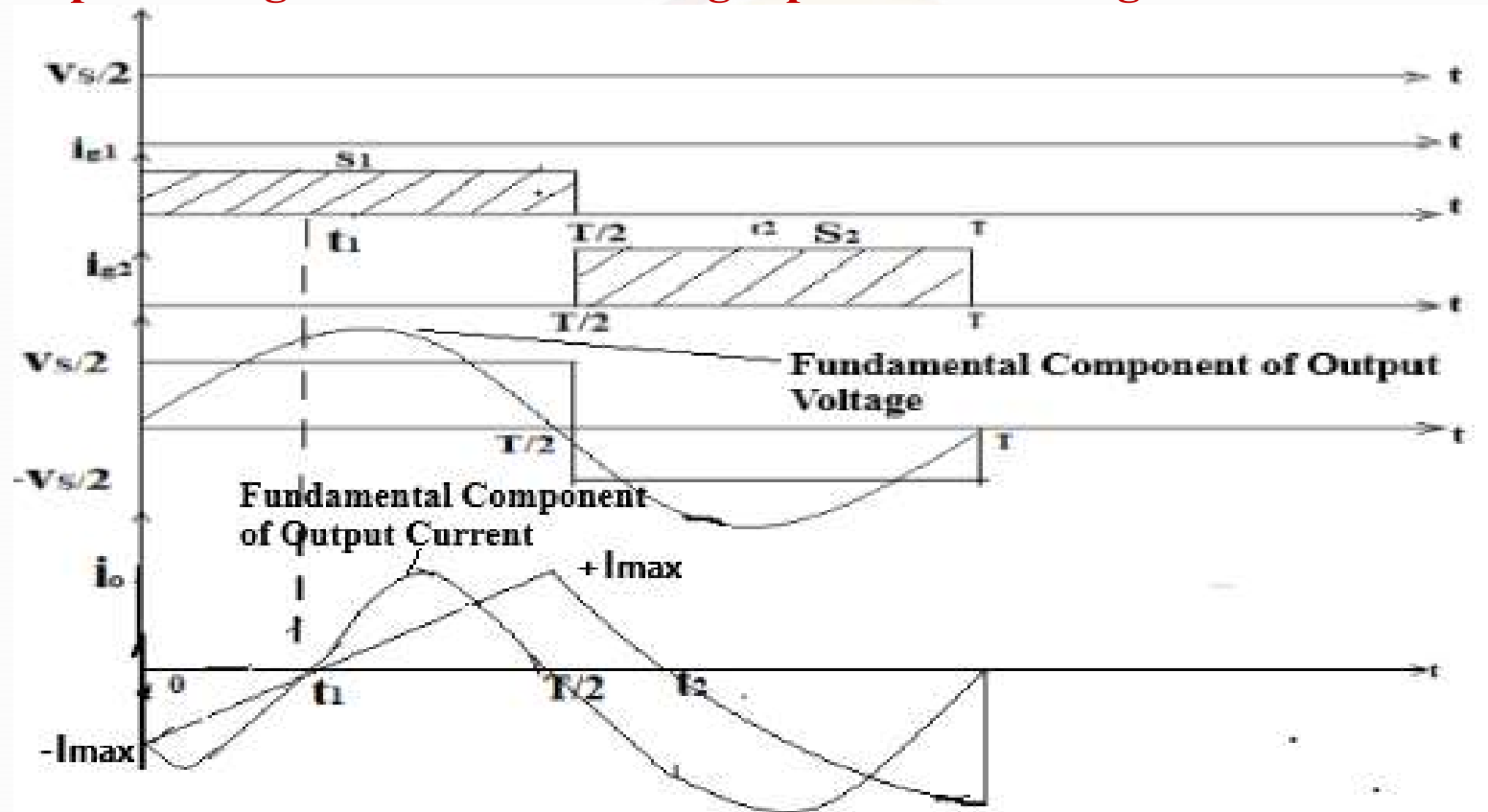The output voltage waveform of a single-phase half-bridge inverter with RL load



School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

Half Bridge Inverter Vs Full Bridge Inverter

S.NO	Half Bridge Inverter	Full Bridge Inverter
1	The efficiency is high in half-bridge inverter	In full-bridge inverter also, the efficiency is high
2	In half-bridge inverter the output voltage waveforms are square, quasi square or PWM	In full-bridge inverter the output voltage waveforms are square, quasi square or PWM
3	The peak voltage in the half-bridge inverter is half of the DC supply voltage	The peak voltage in the full-bridge inverter is the same as the DC supply voltage
4	The half-bridge inverter contains two switches	The full-bridge inverter contains four switches
5	The output voltage is $E_0 = E_{DC} / 2$	The output voltage is $E_0 = E_{DC}$
6	The fundamental output voltage is $E_1 = 0.45 E_{DC}$	The fundamental output voltage is $E_1 = 0.9 E_{DC}$
7	This type of inverter generates bipolar voltages	This type of inverter generates monopolar voltages

Name of the Faculty: Saravanan D

Program Name: B.Tech-EE/EEE

Advantages

The advantages of the single-phase half-bridge inverter are

- Circuit is simple
- Cost is low

Disadvantages

The disadvantages of the single-phase half-bridge inverter are

- The TUF (Transformer Utilization Factor) is low
- Efficiency is low

GALGOTIAS
UNIVERSITY

School of Electrical, Electronics and Communication Engineering

Course Code : BTEE3011

Course Name: Power Electronics

Reference:

- All the contents are taken from open source.
- Power Electronics by Dr. PS Bimbhra



GALGOTIAS
UNIVERSITY

Name of the Faculty: Saravanan D

Program Name: B.Tech-EE/EEE